

## 12 – FARADAY

**LESSON 6.3 KIRCHHOFF'S RULES****Check Your Understanding****A.**

- |                               |  |
|-------------------------------|--|
| <u>node</u>                   | 1. A _____ is a point where two or more conductors meet in a circuit.  |
| <u>current</u>                | 2. Components are in series when _____ has a constant value throughout the path.   |
| <u>junction</u>               | 3. Kirchhoff's First Rule is also called Kirchhoff's Current Law (KCL) or the _____ Rule.  |
| <u>junction</u>               | 4. A _____ refers to a point where three or more conductors meet.  |
| <u>equivalent</u>             | 5. The First Rule states that the total charge or current that enters a node or junction is _____ to the charge that leaves the node or junction.                |
| <u>loop</u>                   | 6. A _____ refers to a closed conducting path.   |
| <u>voltage drops</u>          | 7. Kirchhoff's Second Rule states that the net voltage around the loop in any closed loop system is equivalent to the sum of all the _____ within the same loop. |
| <u>branch</u>                 | 8. A _____ connects two junctions.   |
| <u>voltage</u>                | 9. Components are in parallel when a constant _____ is present in the whole circuit.   |
| <u>Conservation of Charge</u> | 10. The _____ states that the algebraic sum of all the currents that pass through a node is equivalent to zero.  |

**B.**

1. Identify the direction of the loop.


**clockwise**

2. Write the equation using the loop rule.

$$-\sum v = 0$$

3. Solve the value of  $I_2$ .

$$I_2 = 5.15$$

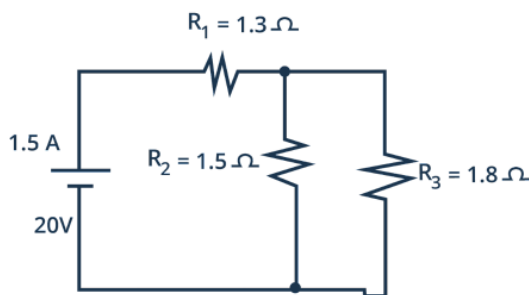

SOLUTION:

$R_1 = 1.3\Omega$   
 $R_2 = 1.5\Omega$   
 $R_3 = 1.8\Omega$   
 $20V$   
 $1.5A$

loop 1:  $V = IR$   
 $+20V - R_1 - R_2 = 0$   
 $+20V - R_1 - I_2 R_2 = 0$   
 $+20V - 1.3I_1 - 1.5I_2 = 0$   
 $+20V = 1.3I_1 + 1.5I_2$   
 $20V = 1.3(I_2 + I_3) + 1.5I_2$   
 $20V = 1.3I_2 + 1.3I_3 + 1.5I_2$   
 $(20V = 2.8I_2 + 1.3I_3)$   
 $360V = 50.4I_2 + 23.4I_3$

loop 2:  $V = IR$   
 $R_2 - R_3 = 0$   
 $I_2 R_2 - I_3 R_3 = 0$   
 $1.5I_2 - 1.8I_3 = 0$   
 $0 = 1.5I_2 - 1.8I_3$   
 $0 = 19.5I_2 - 23.4I_3$

$360V = 50.4I_2 + 23.4I_3$   
 $0V = 19.5I_2 - 23.4I_3$   


---

 $\frac{360V}{69.9} = \frac{69.9I_2}{69.9}$   
 $I_2 = 5.15$

## LESSON 6.4 RC CIRCUITS

### Check Your Understanding

A.

- |                          |  |
|--------------------------|--|
| <u>DC voltage source</u> | 1. An RC circuit contains a resistor and a capacitor that are connected to a _____.  |
| <u>exponential</u>       | 2. There is an _____ time dependence between the capacitor and resistor in an RC circuit.  |
| <u>zero</u>              | 3. In an RC circuit, there is _____ charge in the capacitor prior to charging.   |
| <u>steady state</u>      | 4. In the _____ state of charging a capacitor, the current approaches zero, and the voltage across the resistor becomes equal to the emf across the capacitor. |
| <u>time-dependent</u>    | 5. Lowercase letters $I$ , $v$ , and $q$ are used to signify quantities that are _____.  |

- series 6. RC circuits have a capacitor and a resistor connected in \_\_\_\_\_.
- RC / time constant/ 7. \_\_\_\_\_ is the rate with which the capacitor becomes  
relaxation time charged.  
quicker 8. The smaller  $t$  is, the \_\_\_\_\_ the capacitor charges.  
zero 9. At time  $t=0$ ,  $q=Q$ , the capacitor becomes discharged from the  
resistor, yielding a magnitude of charge equal to \_\_\_\_\_.  
time constant 10. RC is equal to the \_\_\_\_\_ of resistance and capacitance.

B.

Capacitance	Resistance	Time Constant
0.22 $\mu\text{F}$	1. $1.36 \times 10^9 \Omega$	0.5 min
2. $1.79 \times 10^{-3} \text{ F}$	3900 $\Omega$	7s
15pF	6800 $\mu\Omega$	3) $1.02 \times 10^{-13}$
6800 $\mu\text{F}$	4) $0.735 \Omega$	$5 \times 10^{-3} \text{ s}$
5) $0.072 \text{ F}$	1000 $\Omega$	1.2 min

SOLUTION

$$\begin{aligned}
 1. \quad R &= \frac{T}{C} = \frac{0.5 \text{ min}}{0.022 \mu\text{F}} = \frac{30\text{s}}{0.022 \times 10^{-6} \text{ F}} = 1.36 \times 10^9 \Omega \\
 2. \quad C &= \frac{T}{R} = \frac{7\text{s}}{3900 \Omega} = 1.79 \times 10^{-3} \text{ F} \\
 3. \quad T &= RC = (6800 \times 10^{-6} \Omega) (15 \times 10^{-12} \text{ F}) = 1.02 \times 10^{-13} \\
 4. \quad R &= \frac{T}{C} = \frac{5 \times 10^{-3} \text{ s}}{6800 \times 10^{-6} \text{ F}} = 0.735 \Omega \\
 5. \quad C &= \frac{T}{R} = \frac{1.2 \text{ min}}{1000 \Omega} = \frac{72\text{s}}{1000 \Omega} = 0.072
 \end{aligned}$$